
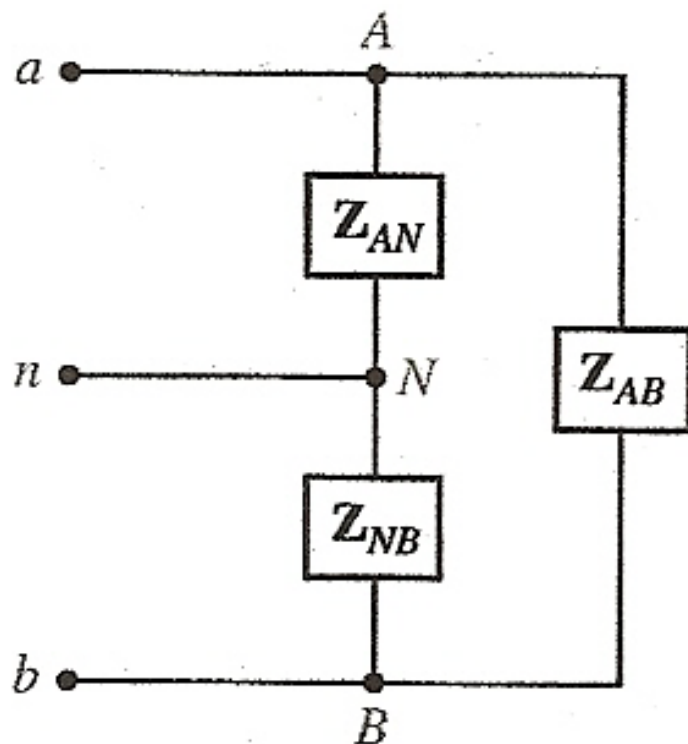


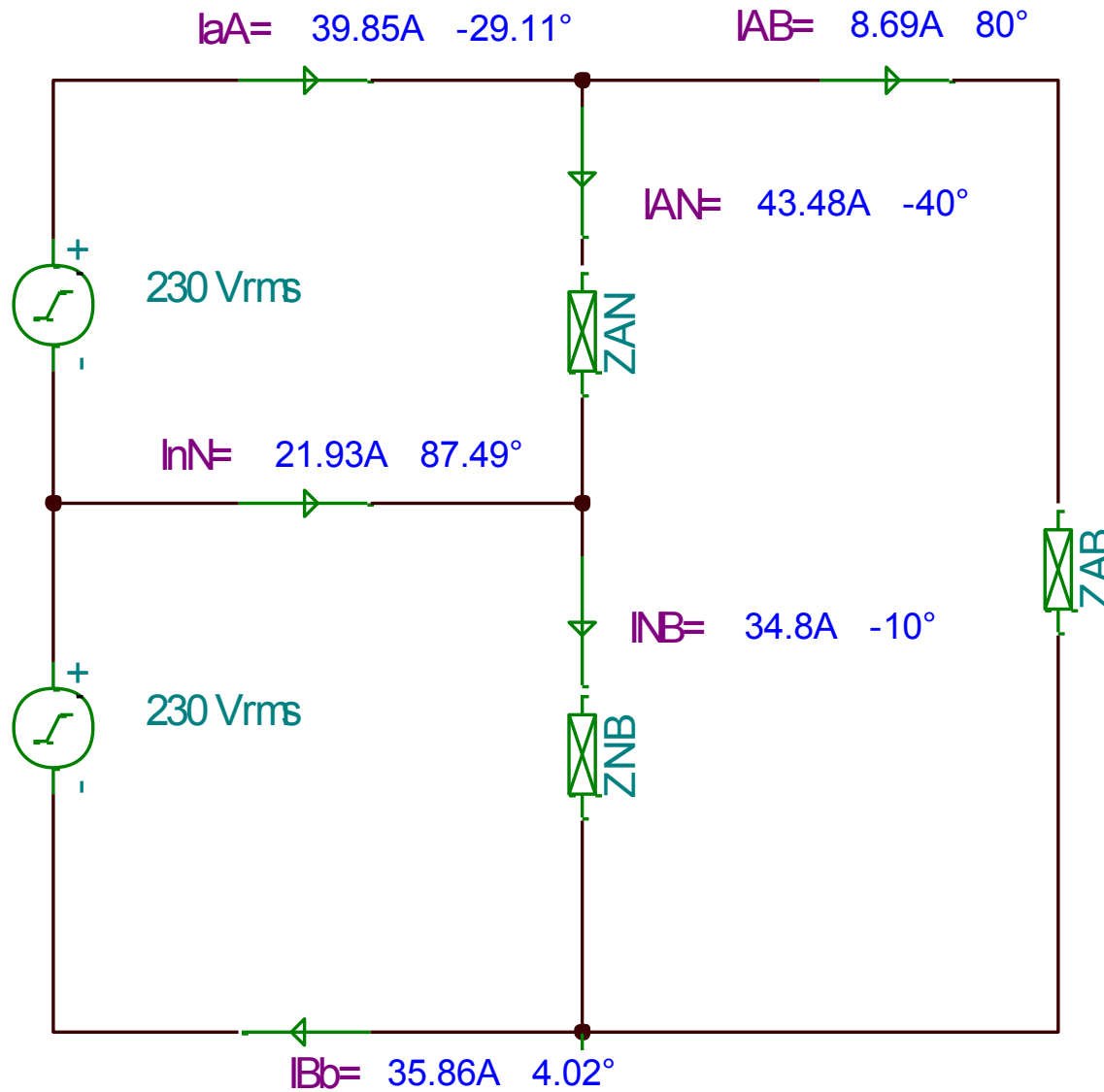
10. The 230/460 V rms 60 Hz three-wire system shown in Fig. 12.29 supplies power to three loads: load  $AN$  draws a complex power of  $10/\underline{40^\circ}$  kVA, load  $NB$  uses  $8/\underline{10^\circ}$  kVA, and load  $AB$  requires  $4/\underline{-80^\circ}$  kVA. Find the two line currents and the neutral current.




## Simulación problema 12.10



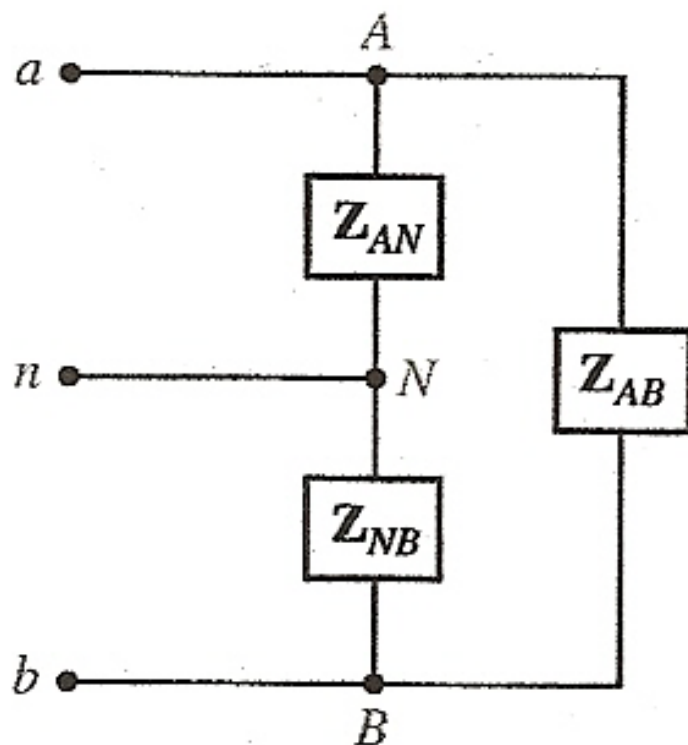
11. A balanced three-wire single-phase system has loads  $Z_{AN} = Z_{NB} = 10 \Omega$ , and a load  $Z_{AB} = 16 + j12 \Omega$ . The three lines may be assumed to be resistanceless. Let  $V_{an} = V_{nb} = 120/0^\circ$  V. (a) Find  $I_{aA}$  and  $I_{nN}$ . (b) The system is unbalanced by connecting another  $10 \Omega$  resistance in parallel with  $Z_{AN}$ . Find  $I_{aA}$ ,  $I_{bB}$ , and  $I_{nN}$ .




## Simulación problema 12.11

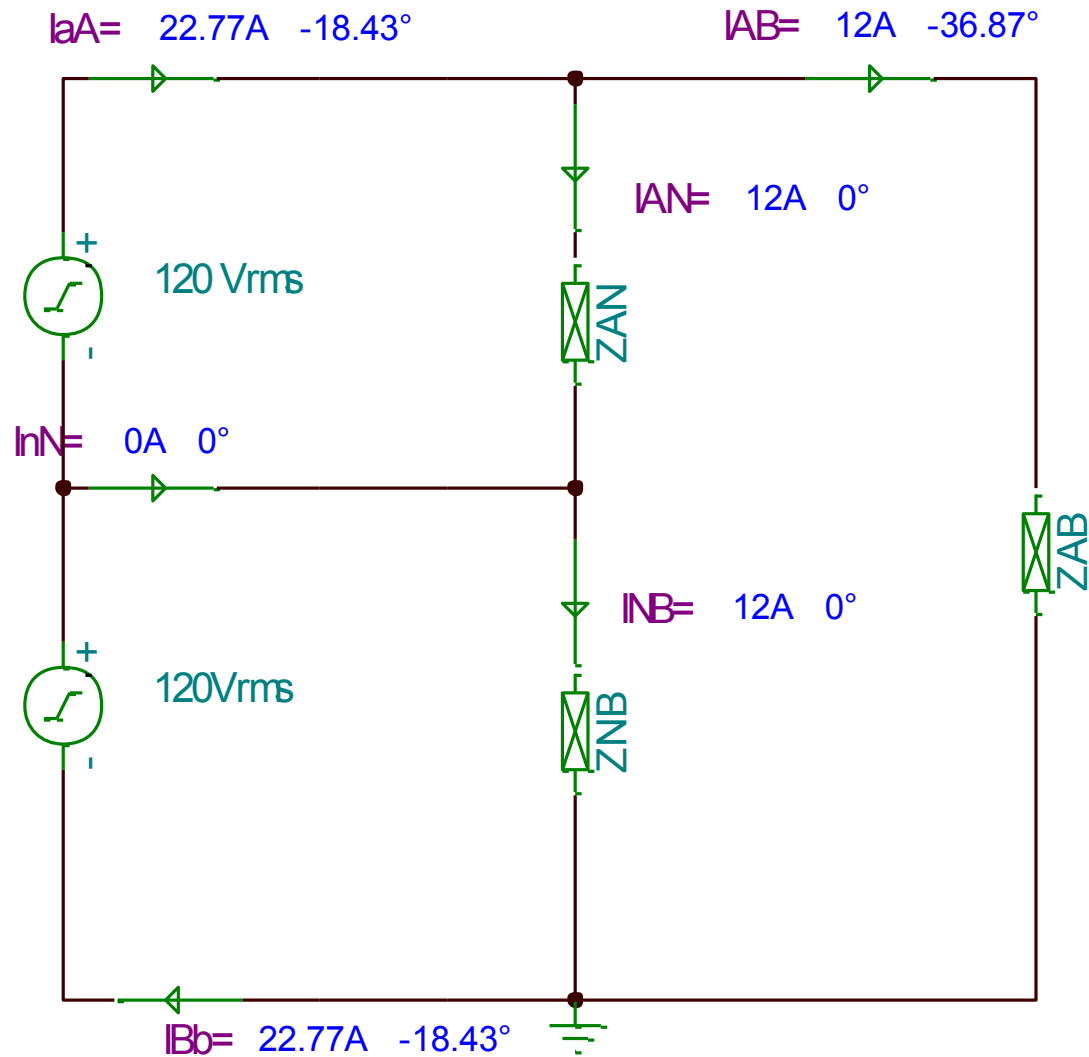

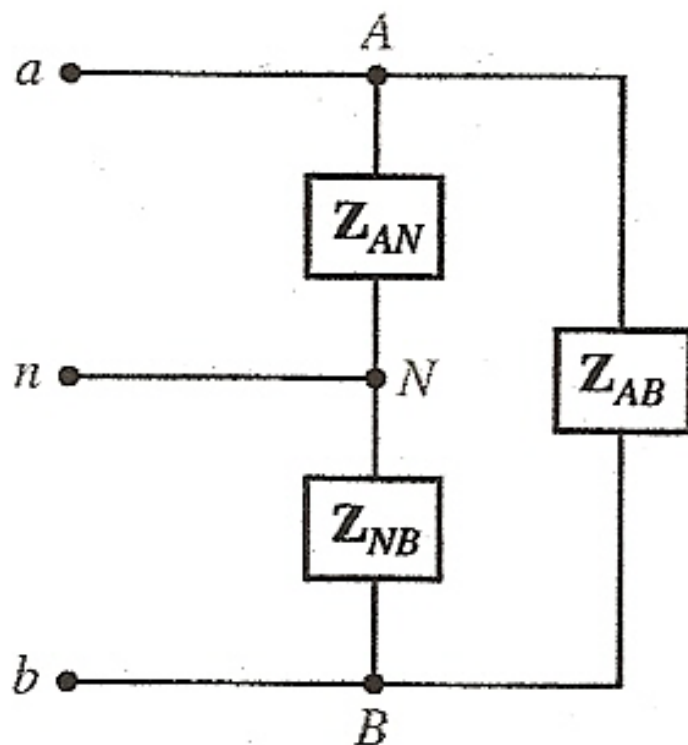
12. An inefficient three-wire single-phase system has source voltages of  $V_{an} = V_{nb} = 720/0^\circ$  V, line resistances  $R_{aA} = R_{bB} = 1\ \Omega$  with  $R_{nN} = 10\ \Omega$ , and loads  $Z_{AN} = 10 + j3\ \Omega$ ,  $Z_{NB} = 8 + j2\ \Omega$ , and  $Z_{AB} = 18 + j0\ \Omega$ . Find (a)  $I_{aA}$ ; (b)  $I_{nN}$ ; (c)  $P_{\text{wiring, total}}$ ; (d)  $P_{\text{gen. total}}$ .



# Simulación

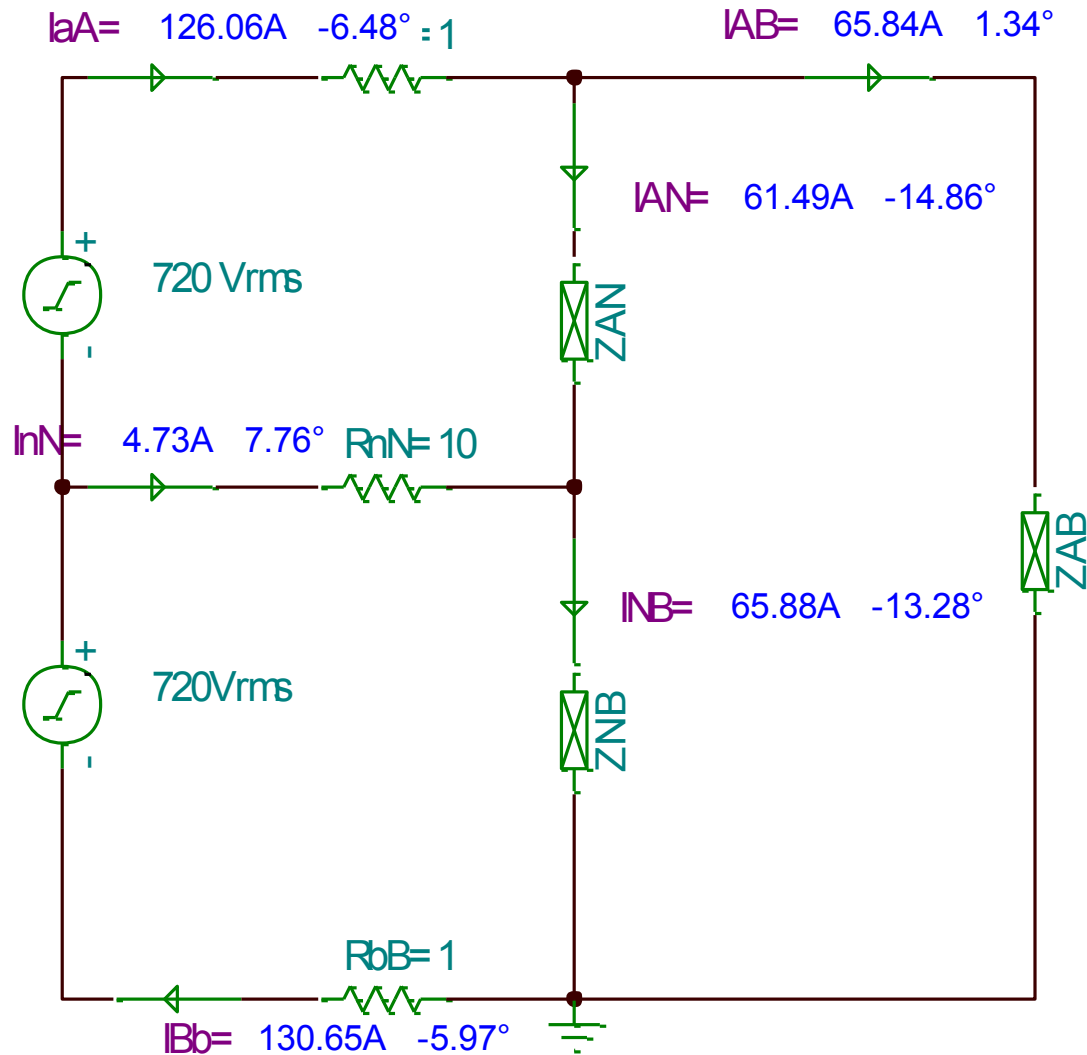


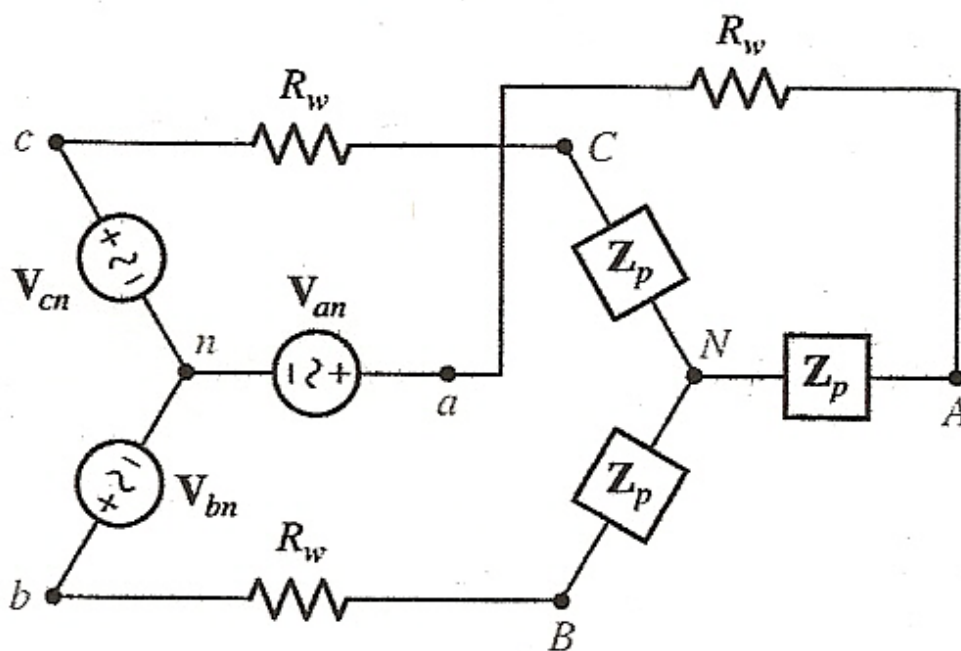15. Figure 12.31 shows a balanced three-phase three-wire system with positive phase sequence. Let  $V_{BC} = 120/60^\circ$  V and  $R_w = 0.6 \Omega$ . If the total load (including wire resistance) draws 5 kVA at PF = 0.8 lagging, find (a) the total power lost in the line resistance, and (b)  $V_{an}$ .



■ FIGURE 12.31
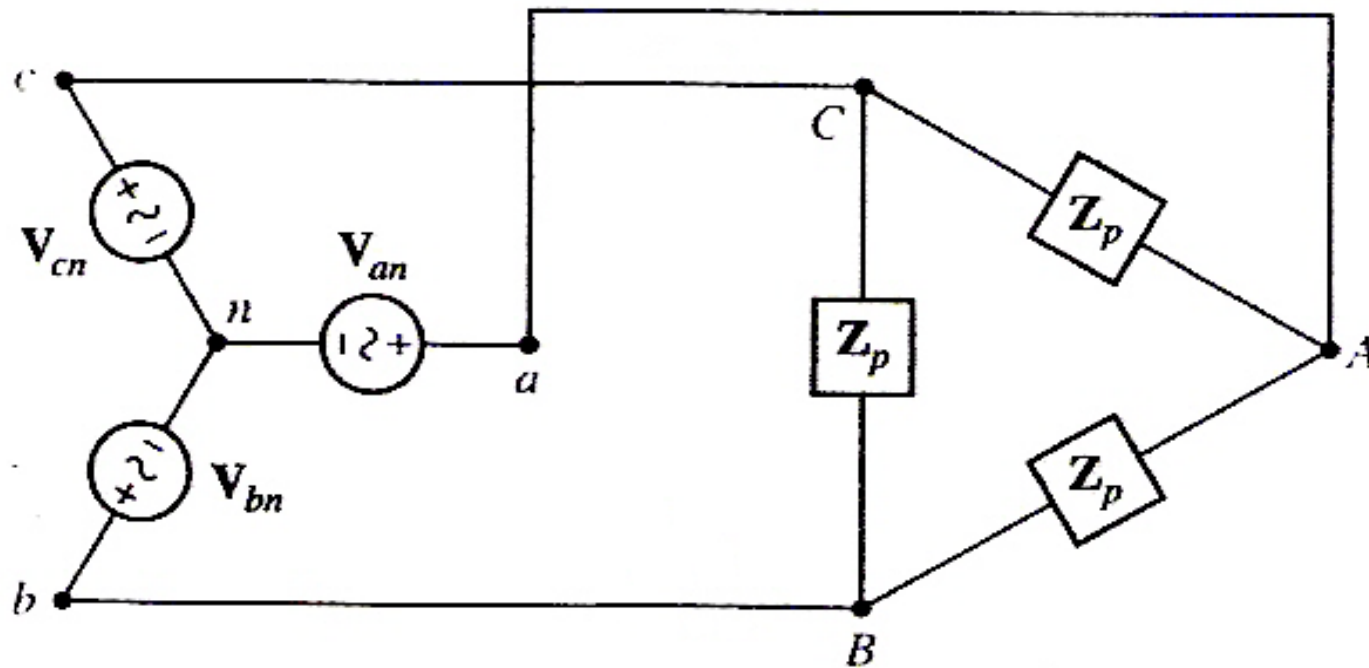
## Conexión estrella delta (Y- $\Delta$ )






### Problema 12.22

La carga conectada en delta ( $\Delta$ ) del circuito de la requiere 15 kVA con un FP retrasado de 0.8. Suponga una secuencia de fase positiva con:


$V_{BC} = 180 \angle 30^\circ$  V. Si  $R_w = 0 \Omega$ , calcule:

a)  $V_{bc}$ ,

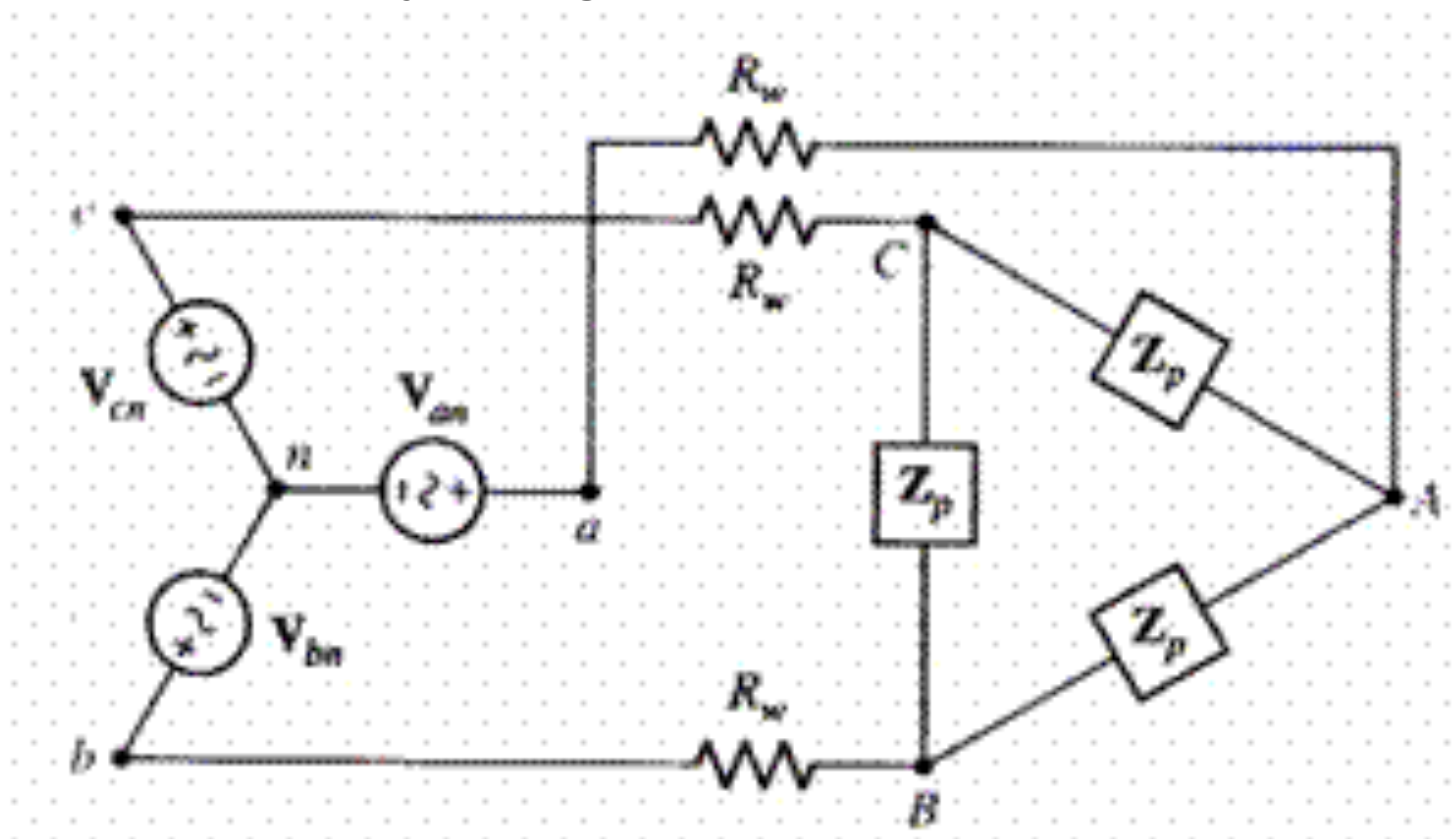b) la potencia compleja total generada por la fuente.




26. The balanced  $\Delta$  load of Fig. 12.32 requires 15 kVA at a lagging PF of 0.8. Assume (+) phase sequence with  $V_{BC} = 180/30^\circ$  V. If  $R_w = 0.75 \Omega$ , find (a)  $V_{bc}$ ; (b) the total complex power generated by the source.

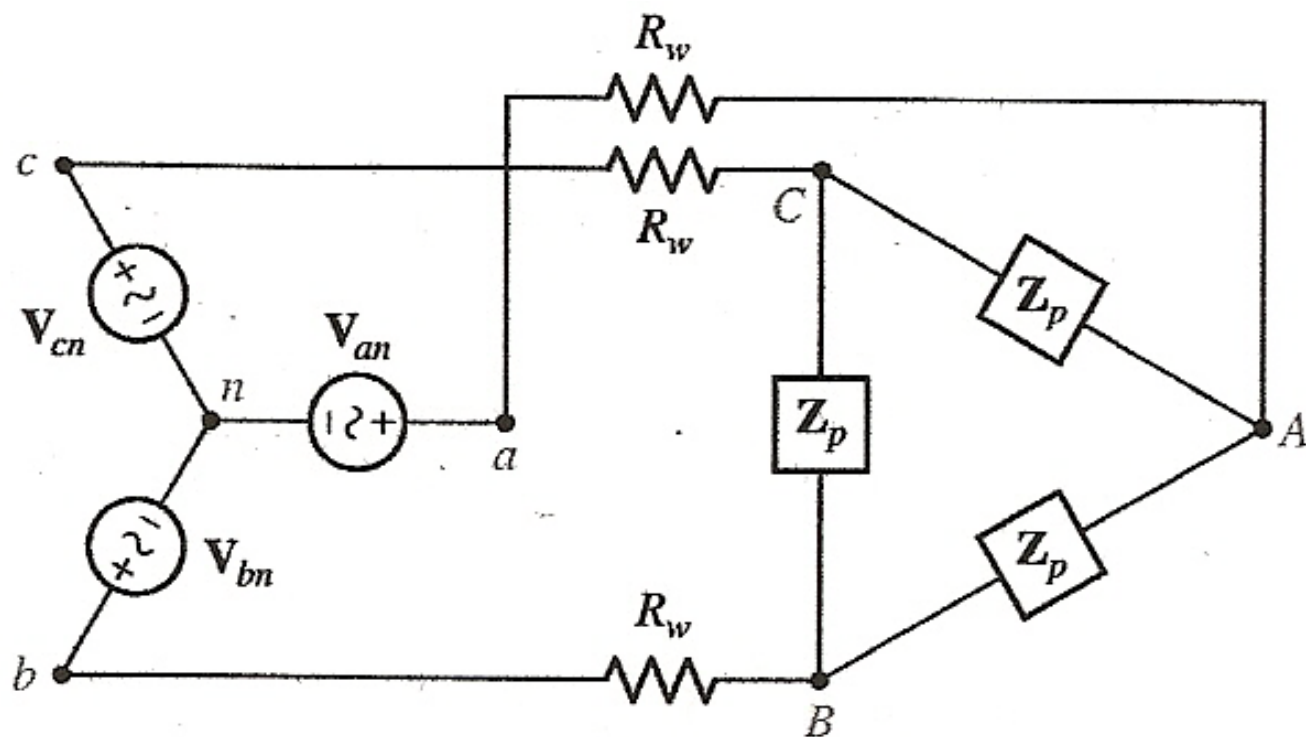


**FIGURE 12.32**

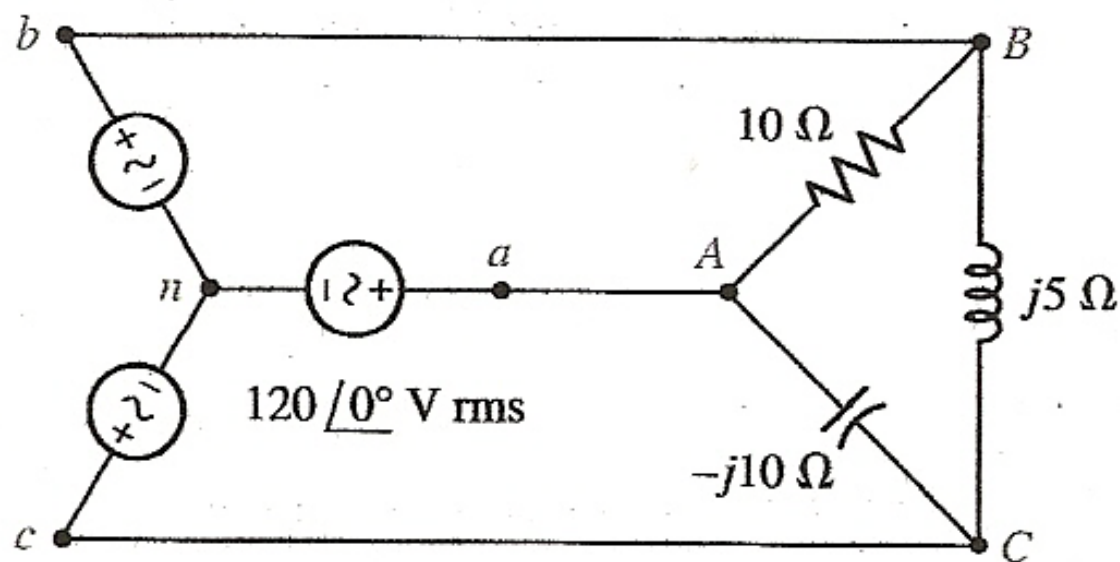29. The source in Fig. 12.33 is balanced and exhibits (+) phase sequence. Find (a)  $I_{aA}$ ; (b)  $I_{bB}$ ; (c)  $I_{cC}$ ; (d) the total complex power supplied by the source.



■ **FIGURE 12.33**

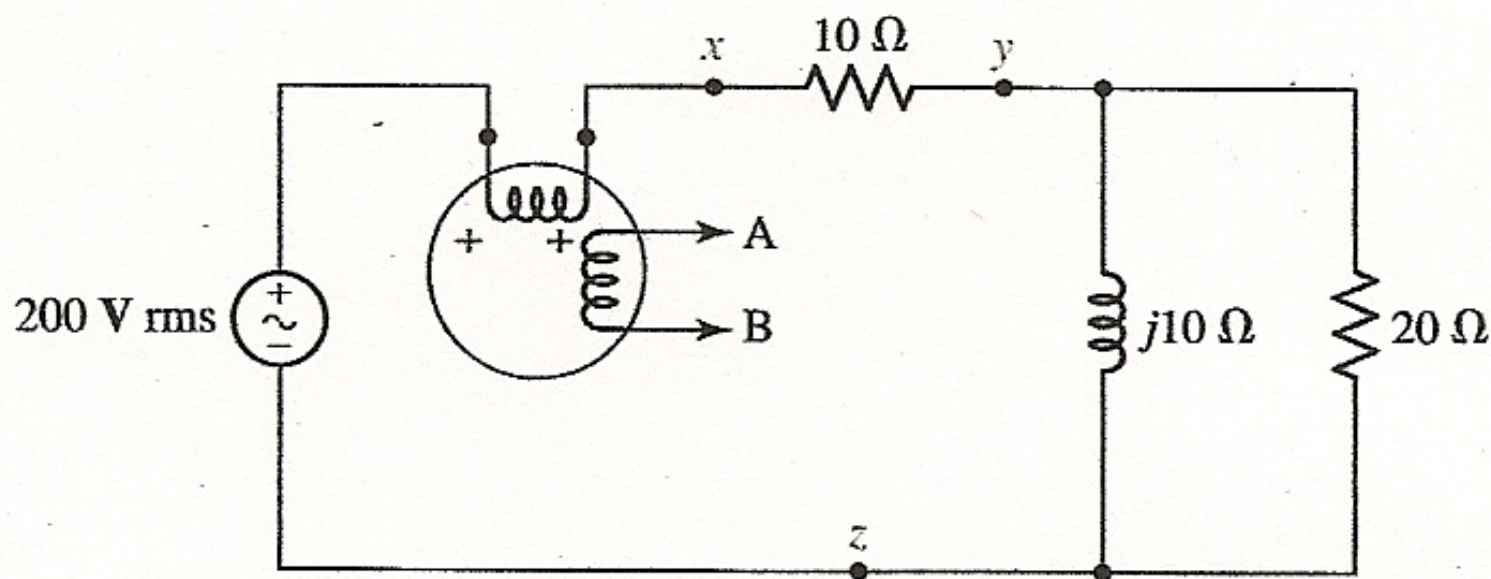35. Determine the wattmeter reading (stating whether or not the leads had to be reversed to obtain it) in the circuit of Fig. 12.35 if terminals  $A$  and  $B$ , respectively, are connected to (a)  $x$  and  $y$ ; (b)  $x$  and  $z$ ; (c)  $y$  and  $z$ .



■ FIGURE 12.35

## Ejemplo


Sean las cargas

$$\mathbf{Z}_A = 25 \angle 60^\circ \, \Omega, \mathbf{Z}_B = 50 \angle -60^\circ \, \Omega, \mathbf{Z}_C = 50 \angle 60^\circ \, \Omega,$$

$$\mathbf{V}_{AB} = 600 \angle 0^\circ \text{ Vrms}$$


con secuencia de fase positiva (+), y el punto  $x$  se ubica en la fase C.

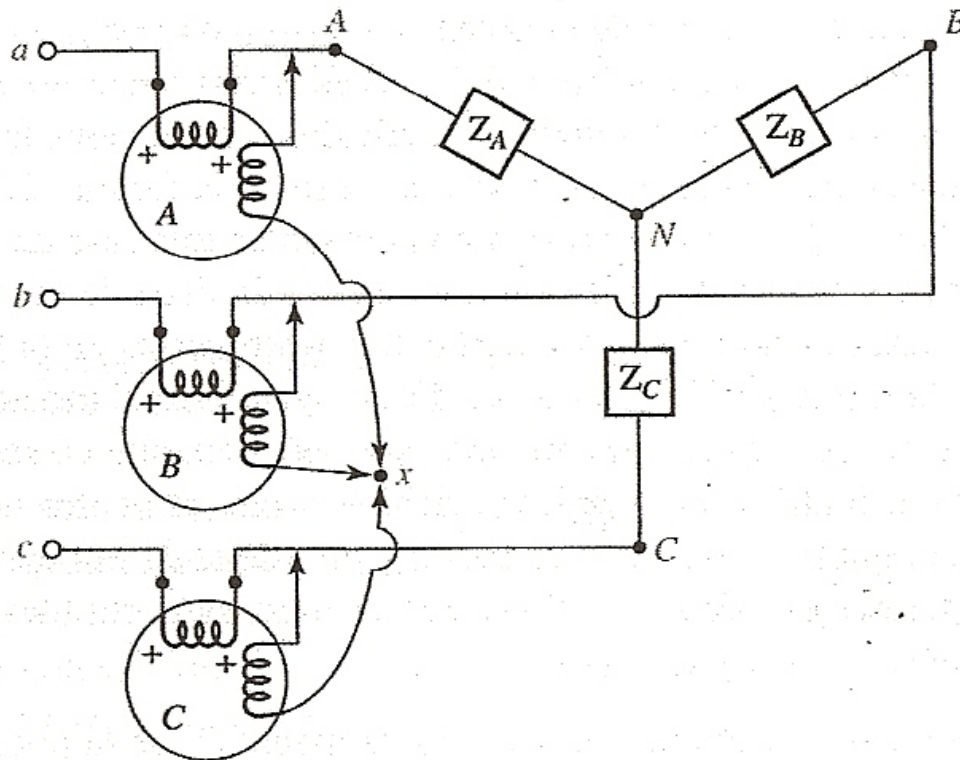Determine las lecturas de los 3 wattímetros ( $P_A, P_B, P_C$ ).






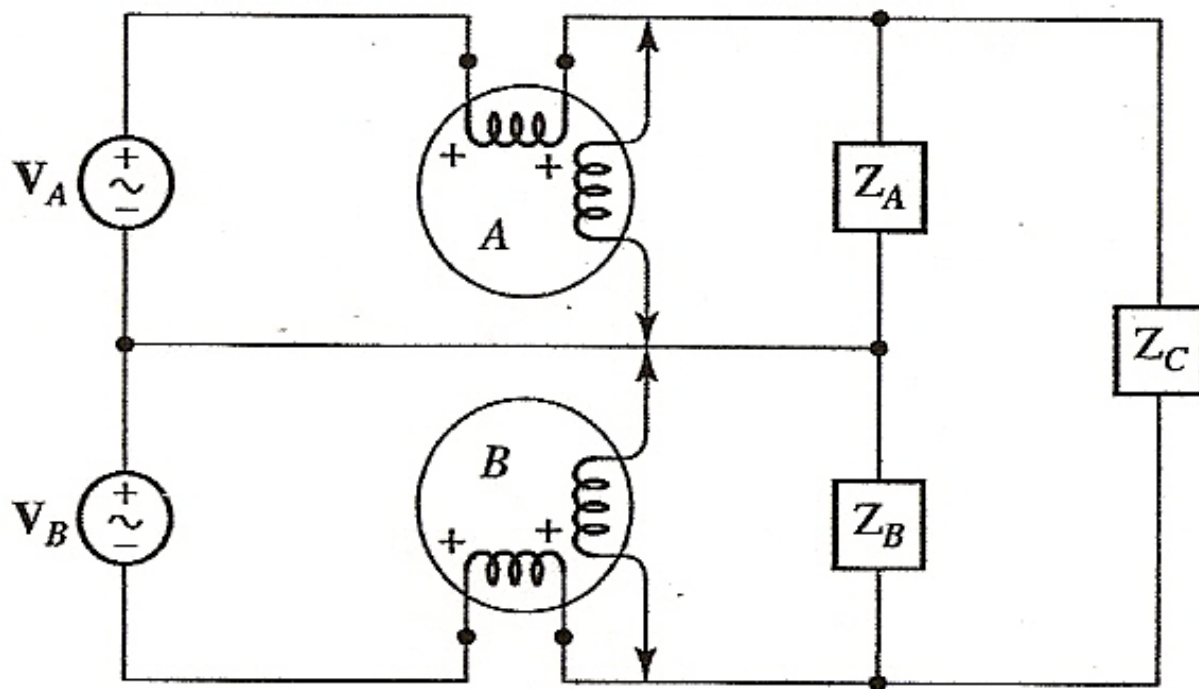58. (a) Find both wattmeter readings in Fig. 12.38 if  $V_A = 100/\underline{0^\circ}$  V rms,  $V_B = 50/\underline{90^\circ}$  V rms,  $Z_A = 10 - j10 \Omega$ ,  $Z_B = 8 + j6 \Omega$ , and  $Z_C = 30 + j10 \Omega$ . (b) Is the sum of these readings equal to the total power taken by the three loads? Verify your answer with an appropriate PSpice simulation.



■ **FIGURE 12.38**

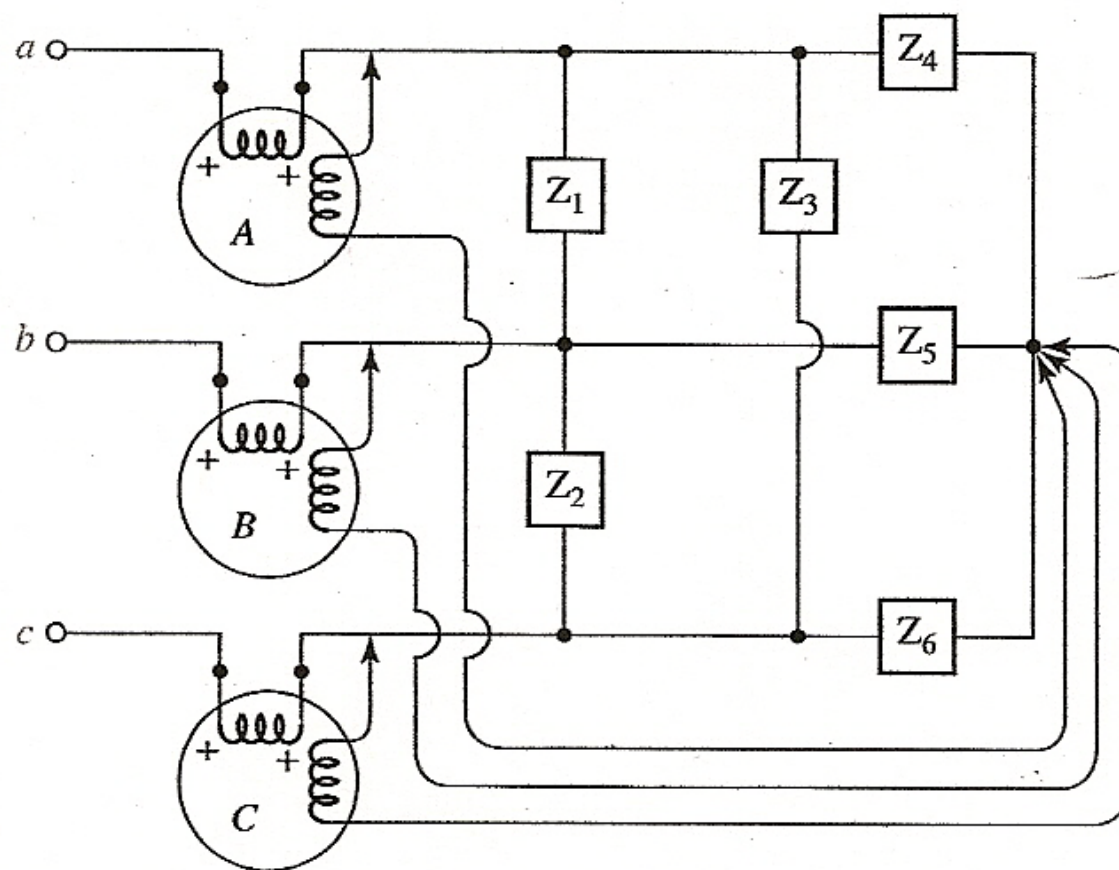39. Circuit values for Fig. 12.39 are  $V_{ab} = 200/0^\circ$ ,  $V_{bc} = 200/120^\circ$ ,  $V_{ca} = 200/240^\circ$  V rms,  $Z_4 = Z_5 = Z_6 = 25/30^\circ \Omega$ ,  $Z_1 = Z_2 = Z_3 = 50/-60^\circ \Omega$ . Find the reading for each wattmeter.



■ FIGURE 12.39